



# آزمایشگاه معماری کامپیوتر آزمایش دوم دکتر محبتی

عرشیا آرین نژاد، حوریه سبزواری، الناز رضایی


فروردین ۱۴۰۱

## هدف آزمایش:

در این آزمایش با المان های نگهدارنده حساس به سطح و لبه مانند T و JK و D فلیپ فلاپ آشنا شدیم. همچنین نحوه نوشتن TESTBENCH و نحوه صحت سنجی کد خود را یاد گرفتیم.

## D Flip Flop:

طراحی شماتیک طرح به صورت فیزیکی:

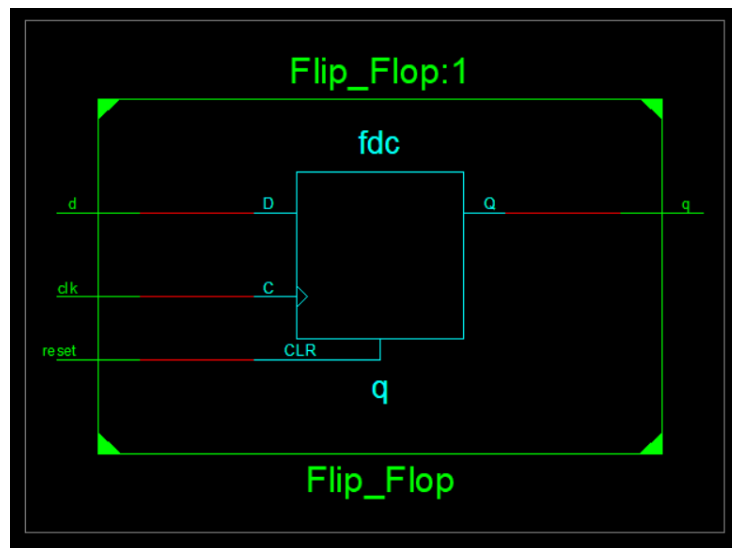

پیاده‌سازی مدارها با استفاده از زبان‌های توصیف:

```
32 entity Flip_Flop is
33     Port ( d : in  STD_LOGIC;
34           reset : in  STD_LOGIC;
35           clk : in  STD_LOGIC;
36           q : out  STD_LOGIC);
37 end Flip_Flop;
38
39 architecture Behavioral of Flip_Flop is
40
41 begin
42     q<='0' when reset = '1' else
43     d when clk'event and clk = '1';
44
45 end Behavioral;
```


## Testbench:

```
35 ENTITY Simulate IS
36 END Simulate;
37
38 ARCHITECTURE behavior OF Simulate IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT Flip_Flop
43     PORT(
44         d : IN  std_logic;
45         reset : IN  std_logic;
46         clk : IN  std_logic;
47         q : OUT std_logic
48     );
49     END COMPONENT;
50
51
52     --Inputs
53     signal d : std_logic := '0';
54     signal reset : std_logic := '0';
55     signal clk : std_logic := '0';
56
57     --Outputs
58     signal q : std_logic;
59
60     -- Clock period definitions
61     constant clk_period : time := 10 ns;
62
63 BEGIN
64
65     -- Instantiate the Unit Under Test (UUT)
66     uut: Flip_Flop PORT MAP (
67         d => d,
68         reset => reset,
69         clk => clk,
70         q => q
71     );
72
```

```



72
73 -- Clock process definitions
74 clk_process :process
75 begin
76     clk <= '0';
77     wait for clk_period/2;
78     clk <= '1';
79     wait for clk_period/2;
80 end process;
81
82
83 -- Stimulus process
84 stim_proc: process
85 begin
86     -- hold reset state for 100 ns.
87     wait for 100 ns;
88     d <= '1', 'X' after 22 ns, '1' after 24 ns, 'U' after 35 ns , '1' after 40 ns;
89     reset <= '1' after 50 ns , '0' after 60 ns;
90     wait for clk_period*10;
91
92     -- insert stimulus here
93
94     wait;
95 end process;
96
97 END;
98

```

 

## JK Flip Flop:

طراحی شماتیک طرح به صورت فیزیکی:

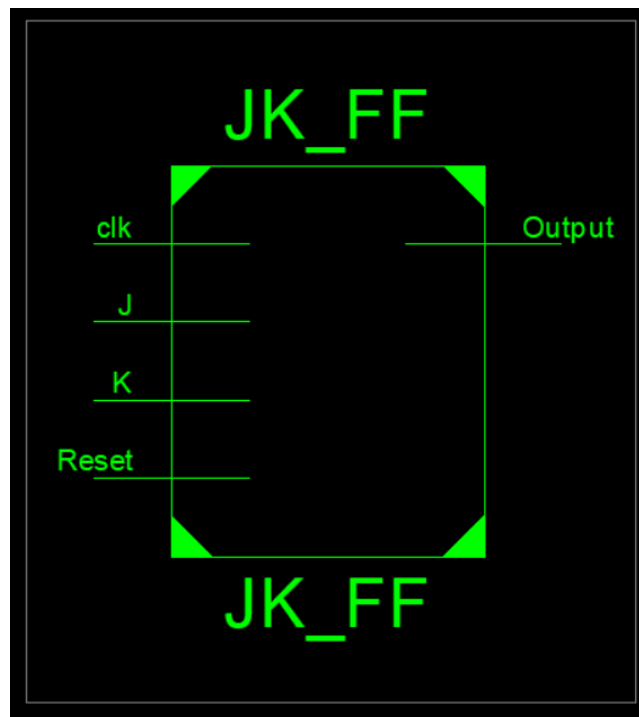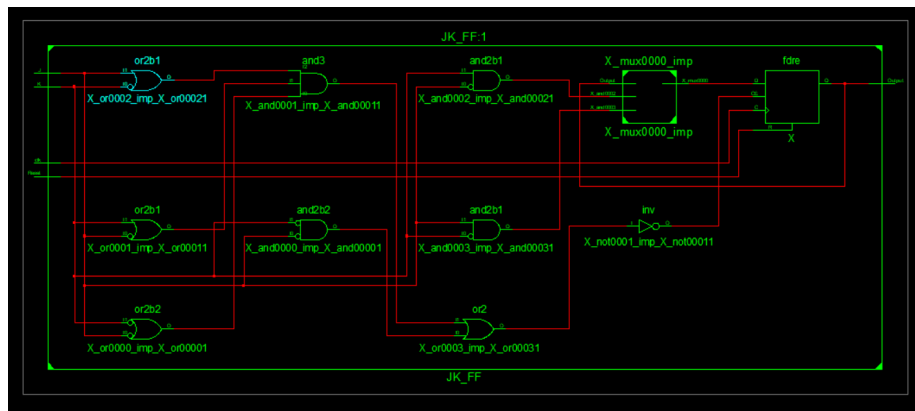

پیاده‌سازی مدارها با استفاده از زبان‌های توصیف:

```
32 entity JK_FF is
33     port( J,K: in  std_logic;
34           Reset: in std_logic;
35           clk: in std_logic;
36           Output: out std_logic);
37 end JK_FF;
38
39 architecture Behavioral of JK_FF is
40     signal X: std_logic;
41 begin
42     process (clk)
43     begin
44         if rising_edge(clk) then
45             if Reset='1' then
46                 X <= '0';
47             else
48                 if (J='0' and K='0') then
49                     X <= X;
50                 elsif (J='0' and K='1') then
51                     X <= '0';
52                 elsif (J='1' and K='0') then
53                     X <= '1';
54                 elsif (J='1' and K='1') then
55                     X <= not (X);
56                 end if;
57             end if;
58         end if;
59     end process;
60     Output <= X;
61
62 end Behavioral;
```

## Testbench:


```
35 ENTITY Simulate IS
36 END Simulate;
37
38 ARCHITECTURE behavior OF Simulate IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT JK_FF
43     PORT(
44         J : IN  std_logic;
45         K : IN  std_logic;
46         Reset : IN  std_logic;
47         clk : IN  std_logic;
48         Output : OUT std_logic
49     );
50     END COMPONENT;
51
52
53     --Inputs
54     signal J : std_logic := '0';
55     signal K : std_logic := '0';
56     signal Reset : std_logic := '0';
57     signal clk : std_logic := '0';
58
59     --Outputs
60     signal Output : std_logic;
61
62     -- clk period definitions
63     constant clk_period : time := 10 ns;
64
65 BEGIN
66
67     -- Instantiate the Unit Under Test (UUT)
68     uut: JK_FF PORT MAP (
69         J => J,
70         K => K,
71         Reset => Reset,
72         clk => clk,
73         Output => Output
74     );
```



```



75
76  -- clk process definitions
77  clk_process :process
78  begin
79      clk <= '0';
80      wait for clk_period/2;
81      clk <= '1';
82      wait for clk_period/2;
83  end process;
84
85
86  -- Stimulus process
87  stim_proc: process
88  begin
89      -- hold reset state for 100 ns.
90      J <= '0';
91      k <= '0';
92      wait for 100 ns;
93      J <= '1';
94      k <= '0';
95      wait for 100 ns;
96      J <= '0';
97      k <= '1';
98      wait for 100 ns;
99      J <= '1';
100     k <= '1';
101     wait for 100 ns;
102     wait for clk_period*10;
103
104     -- insert stimulus here
105
106     wait;
107  end process;
108
109  END;

```

 

## T Flip Flop:

طراحی شماتیک طرح به صورت فیزیکی:

 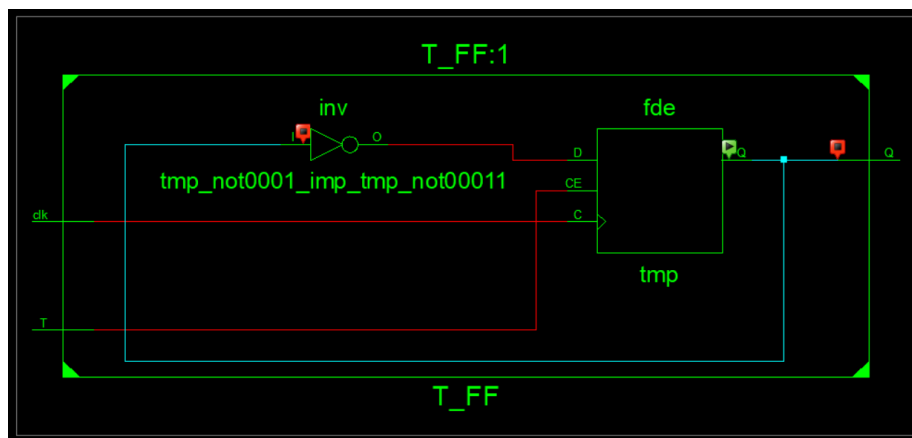

پیاده‌سازی مدارها با استفاده از زبان‌های توصیف:

```
32 entity T_FF is
33     port( T: in std_logic;
34           clk: in std_logic;
35           Q: out std_logic);
36 end T_FF;
37
38 architecture Behavioral of T_FF is
39     signal tmp: std_logic := '0';
40 begin
41     process (clk)
42     begin
43         if clk'event and clk='1' then
44
45             if T='0' then
46                 tmp <= tmp;
47             elsif T='1' then
48                 tmp <= not (tmp);
49             end if;
50         end if;
51     end process;
52     Q <= tmp;
53
54 end Behavioral;
```

## Testbench:

```
35 ENTITY Simulate IS
36 END Simulate;
37
38 ARCHITECTURE behavior OF Simulate IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT T_FF
43     PORT(
44         T : IN  std_logic;
45         clk : IN  std_logic;
46         Q : OUT std_logic
47     );
48     END COMPONENT;
49
50
51     --Inputs
52     signal T : std_logic := '0';
53     signal clk : std_logic := '0';
54
55     --Outputs
56     signal Q : std_logic;
57
58     -- Clock period definitions
59     constant clk_period : time := 10 ns;
60
61 BEGIN
62
63     -- Instantiate the Unit Under Test (UUT)
64     uut: T_FF PORT MAP (
65         T => T,
66         clk => clk,
67         Q => Q
68     );
```

```

69
70  -- Clock process definitions
71  clk_process :process
72  begin
73      clk <= '0';
74      wait for clk_period/2;
75      clk <= '1';
76      wait for clk_period/2;
77  end process;
78
79
80  -- Stimulus process
81  stim_proc: process
82  begin
83      -- hold reset state for 100 ns.
84      T <='0';
85      wait for 100 ns;
86      T <='1';
87      wait for 100 ns;
88      T <='0';
89      wait for 100 ns;
90      T <='1';
91      wait for 100 ns;
92
93      wait for clk_period*10;
94
95      -- insert stimulus here
96
97      wait;
98  end process;
99
100 END;
101

```

